

0306-341 HW #8 Spring 2009

Due Fri 5/15/09

Complete the following questions in the textbook.

14.12, 14.13, 14.16, 14.34

Derive the state tables, state diagrams, equations, and circuits for 14.12 and 14.13. For 14.16 and 14.34, simply derive the state diagrams.

Note that questions 14.4-14.11 all have answer keys at the end of the textbook. I will encourage you to try them and compare your results to the answers.